

Project 1: part 1

CPE 151: CMOS & VLSI

Section 1


Dr. Praveen Meduri

Andrew Stich


3-9-18

Inverter
 $(W/L)_n = (1.8/0.18)$
 $(W/L)_p = (3.6/0.18)$

Schematic (Inverter)

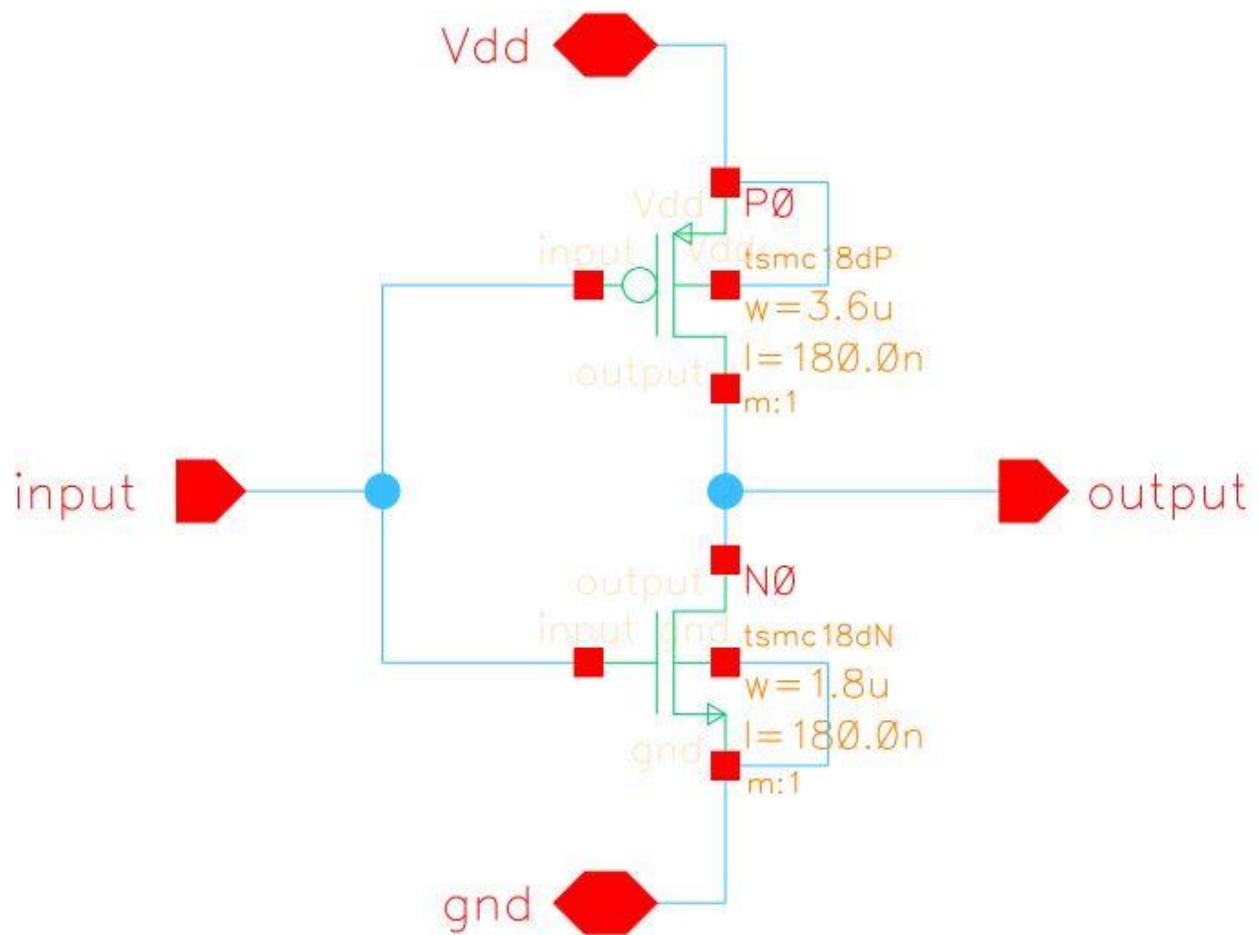

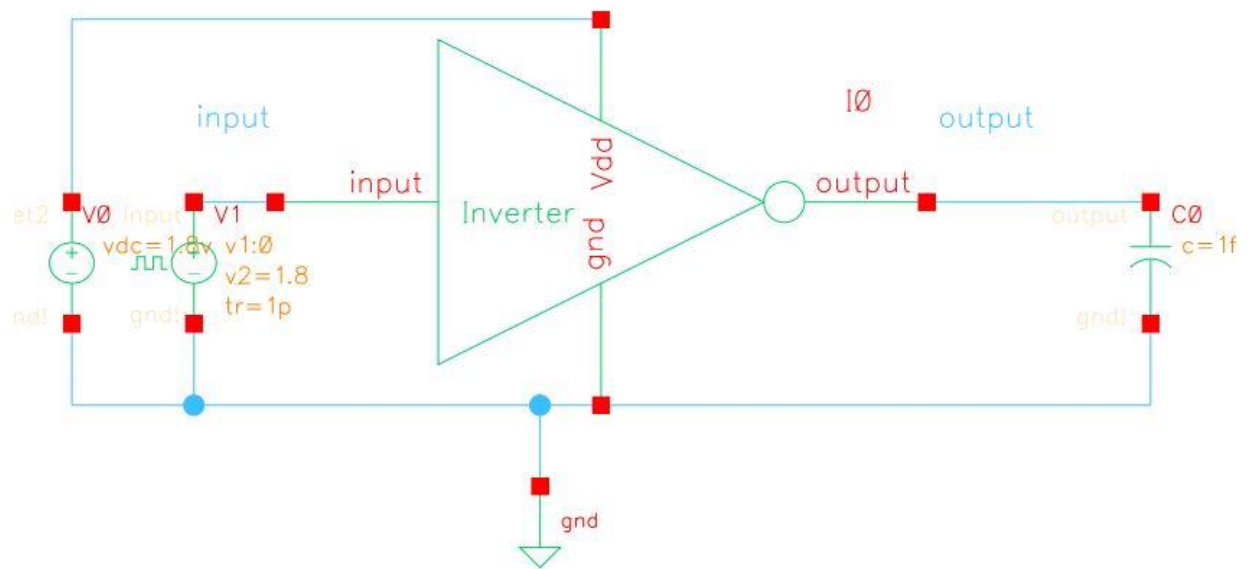
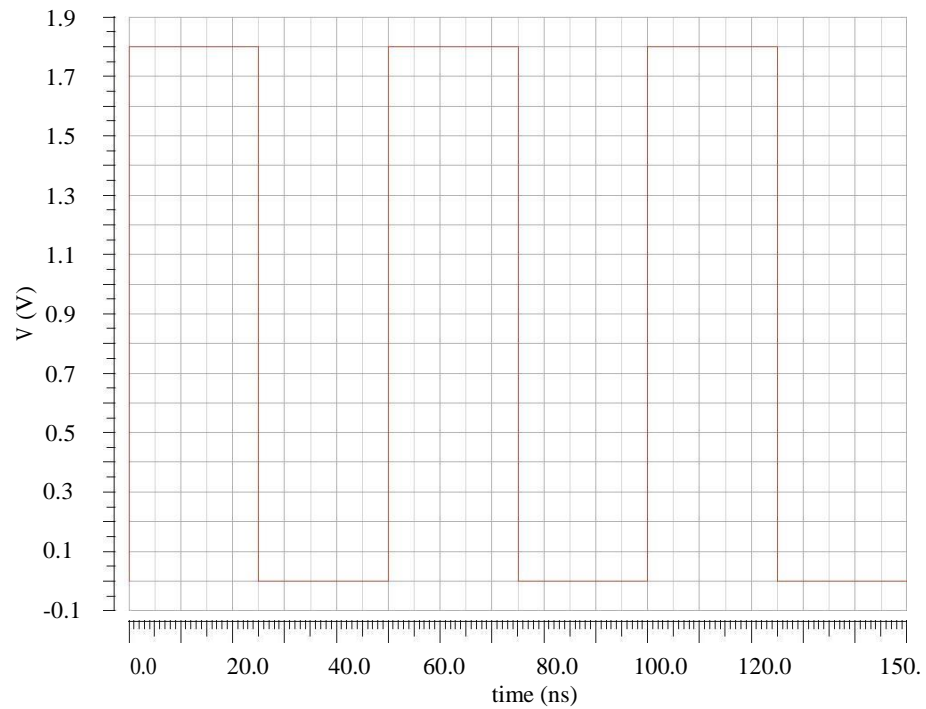
Test-Bench (inverter)



Transient Response


Thu Mar 8 18:41:17 2018

Name	Vis
/input	




Transient Analysis `tran': time = (0 s -> 150 ns)

Name
/output

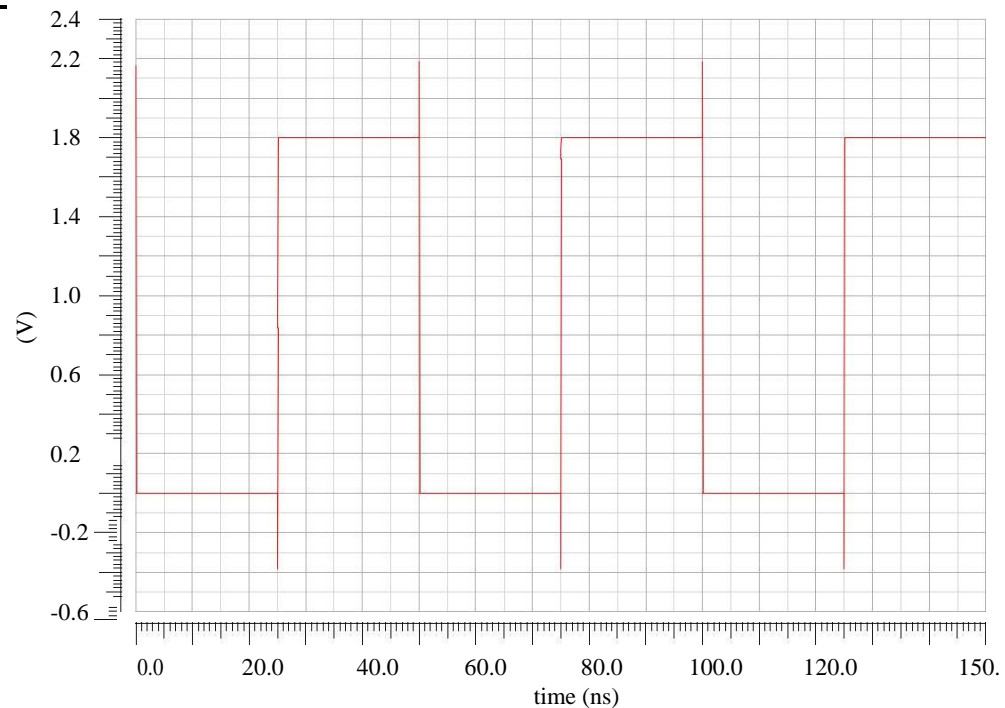


Layout (Inverter)

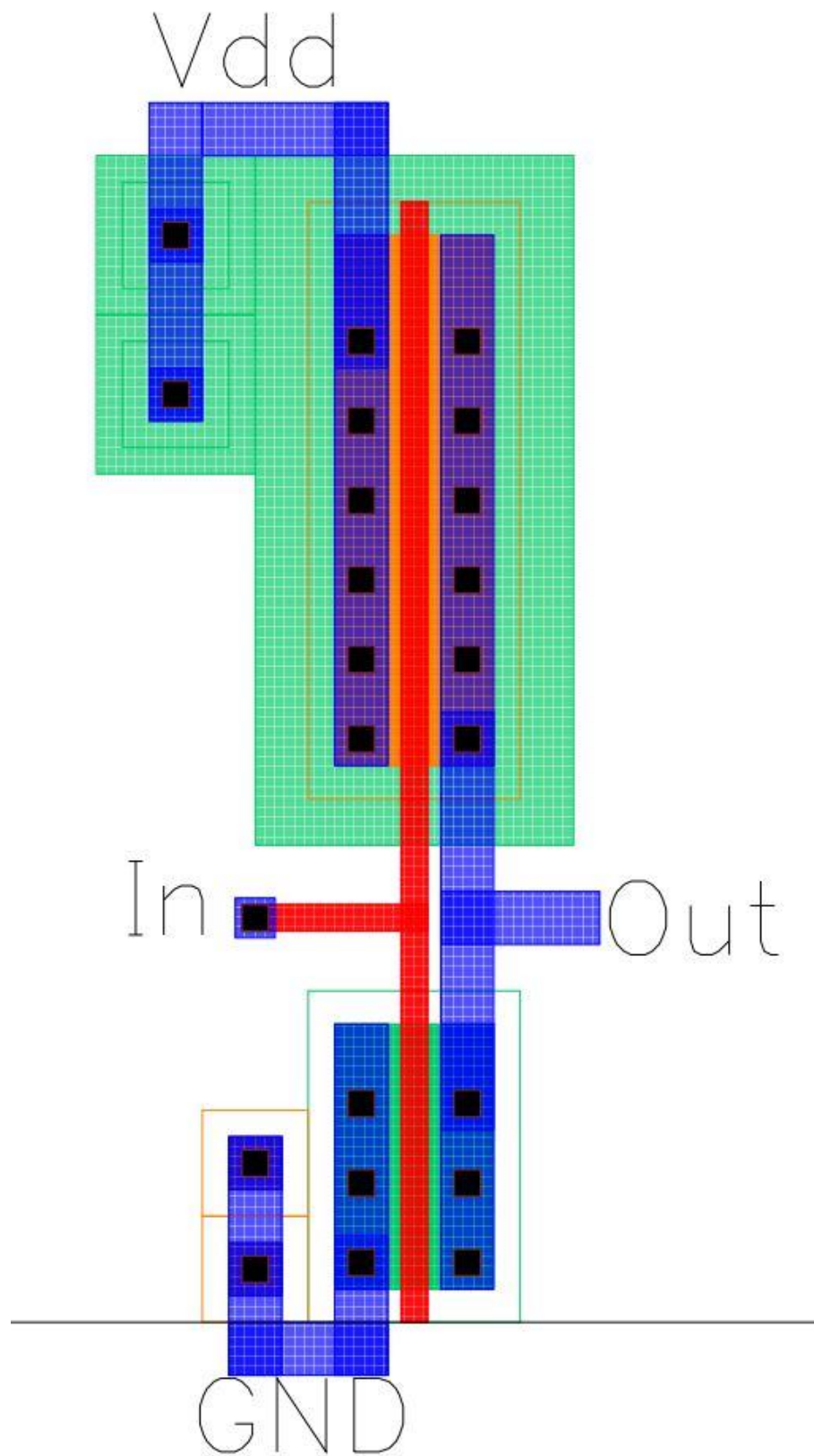


3-Input NAND gate

$(W/L)_n = (5.4/0.18)$
 $(W/L)_p = (3.6/0.18)$

Schematic (NAND)

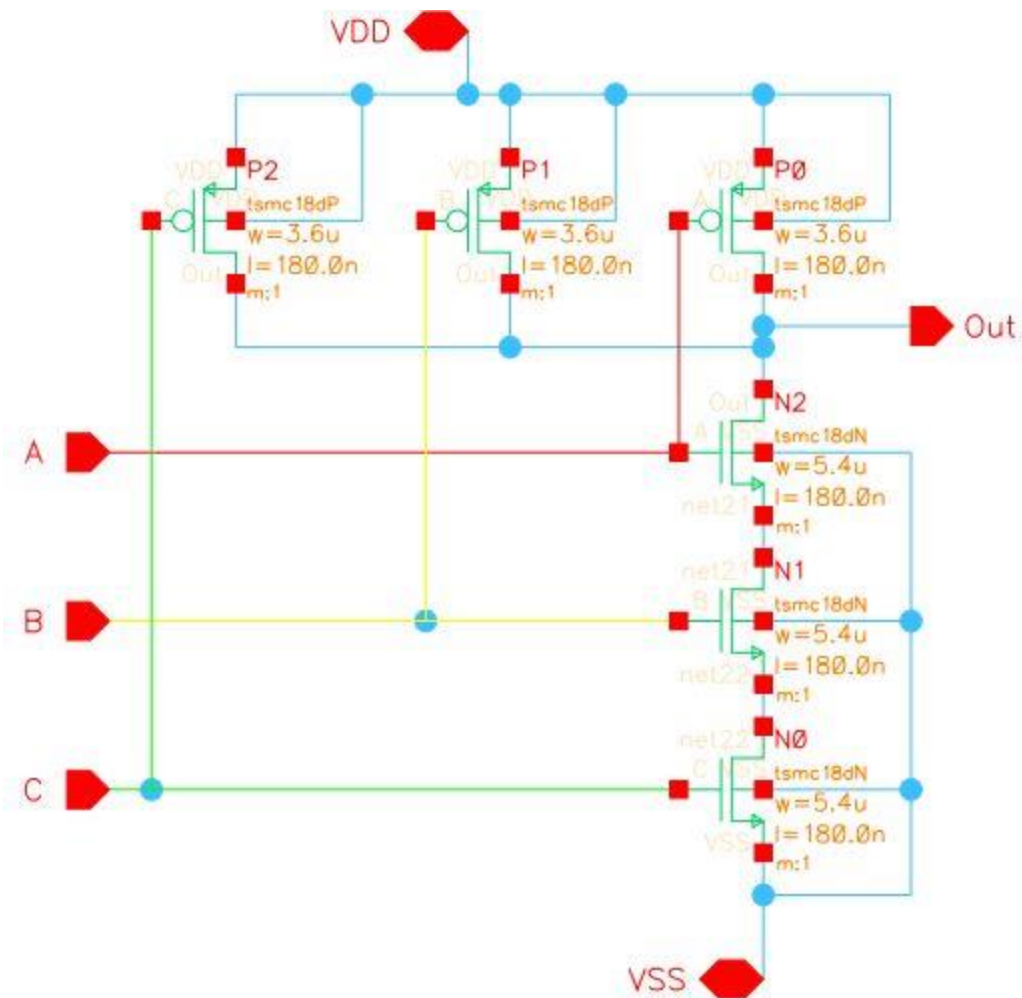


Test-bench (NAND)

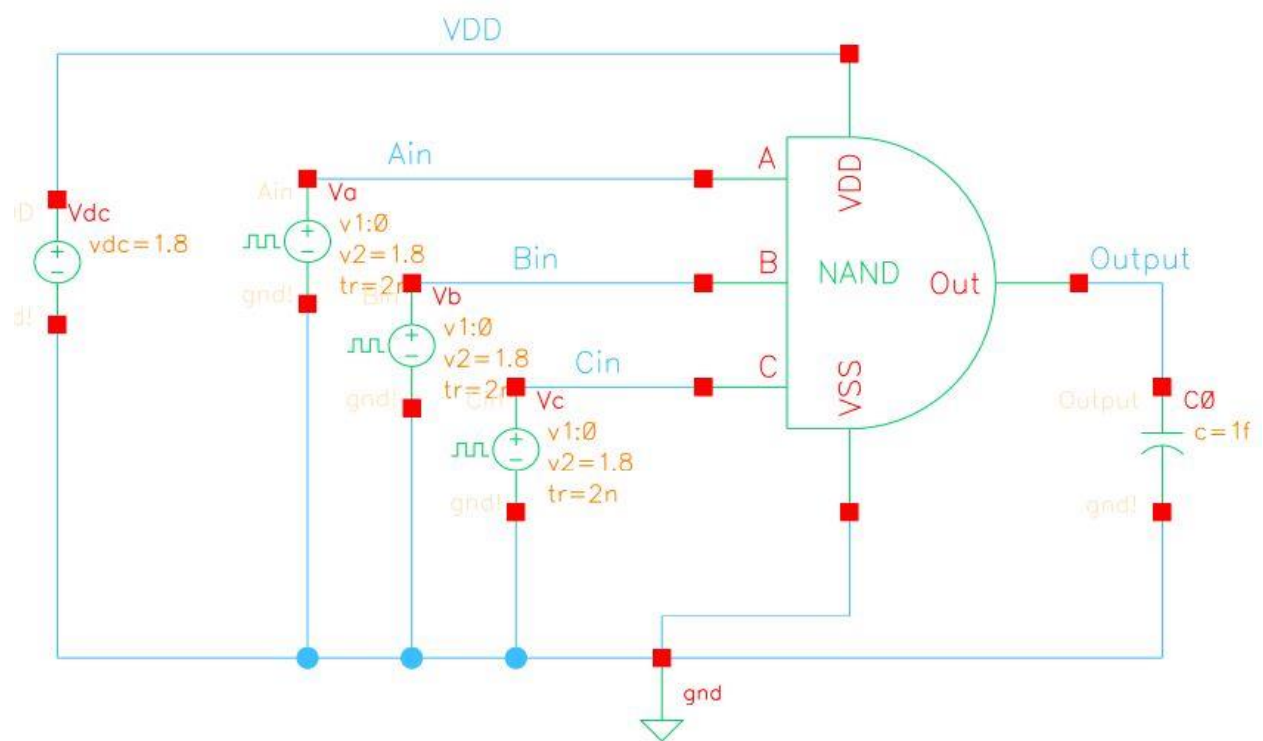


Transient Response

Thu Mar 8 18:31:44 2018

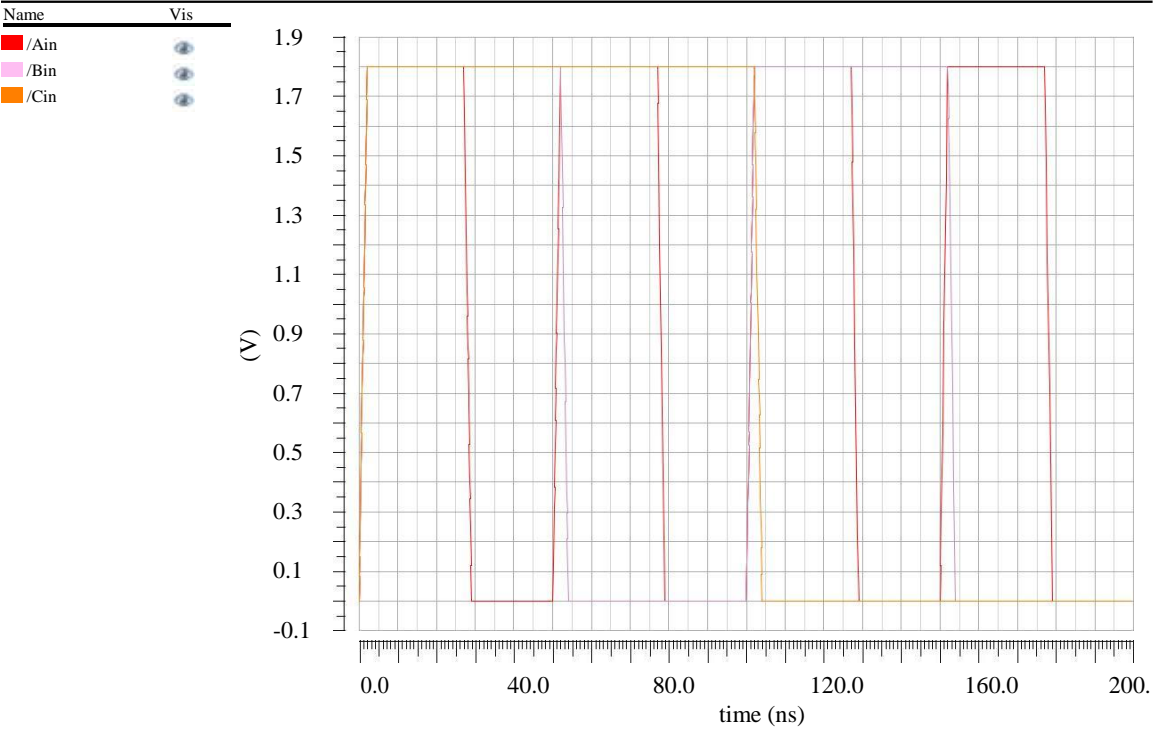


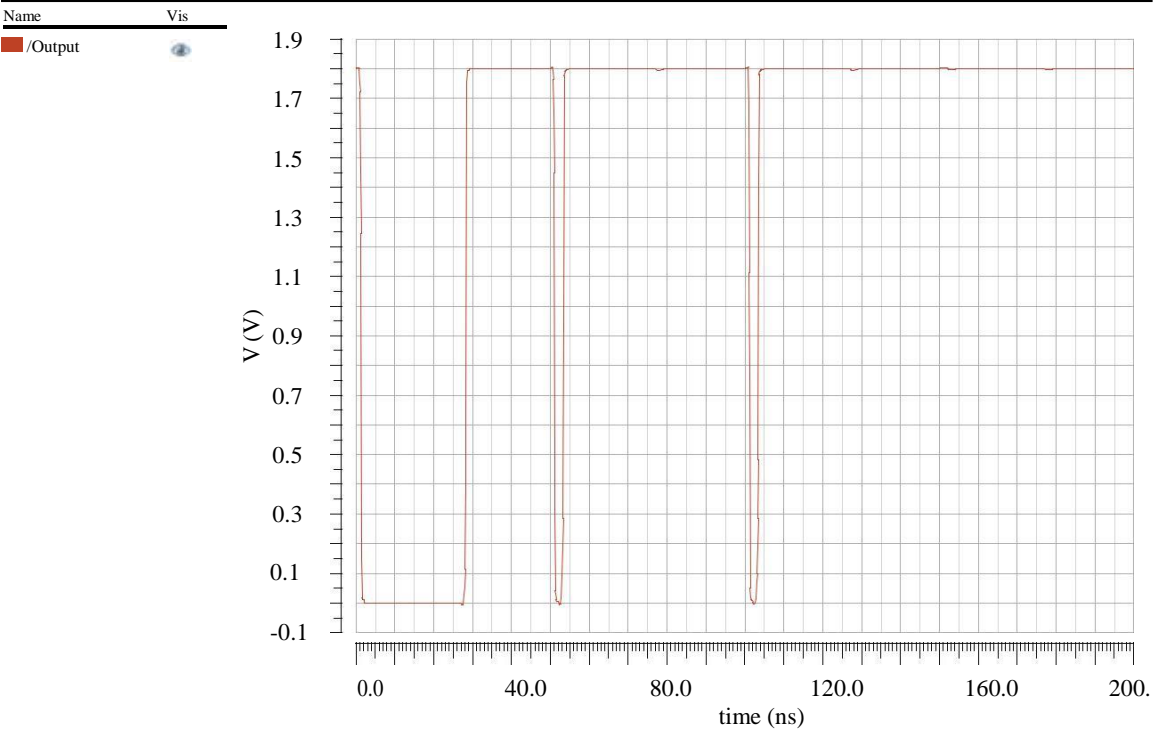Transient Analysis `tran': time = (0 s -> 200 ns)




2 Input NOR gate
 $(W/L)_n = (1.8/0.18)$
 $(W/L)_p = (7.2/0.18)$

Schematic (NOR)

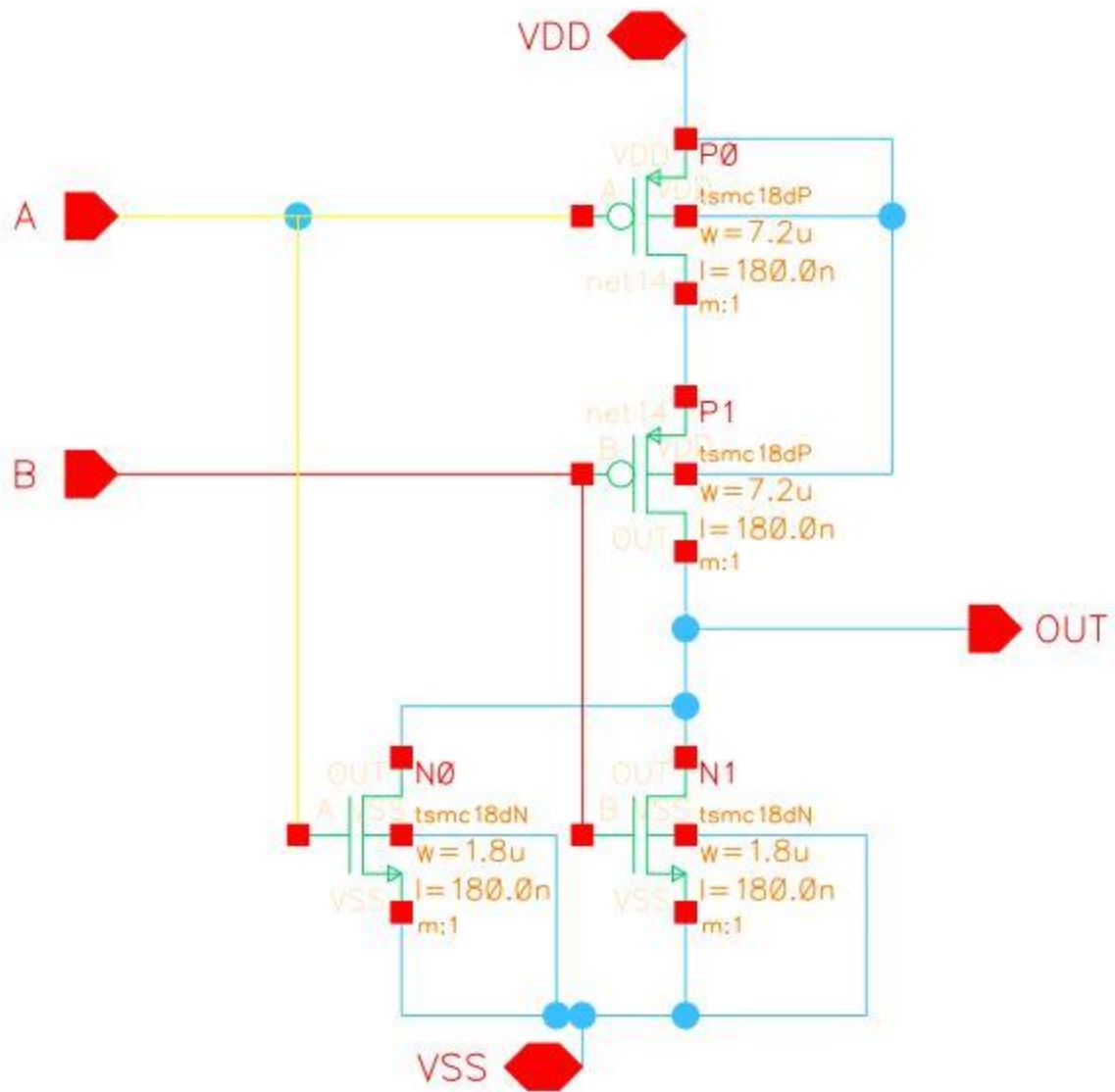

Test-Bench (NOR)

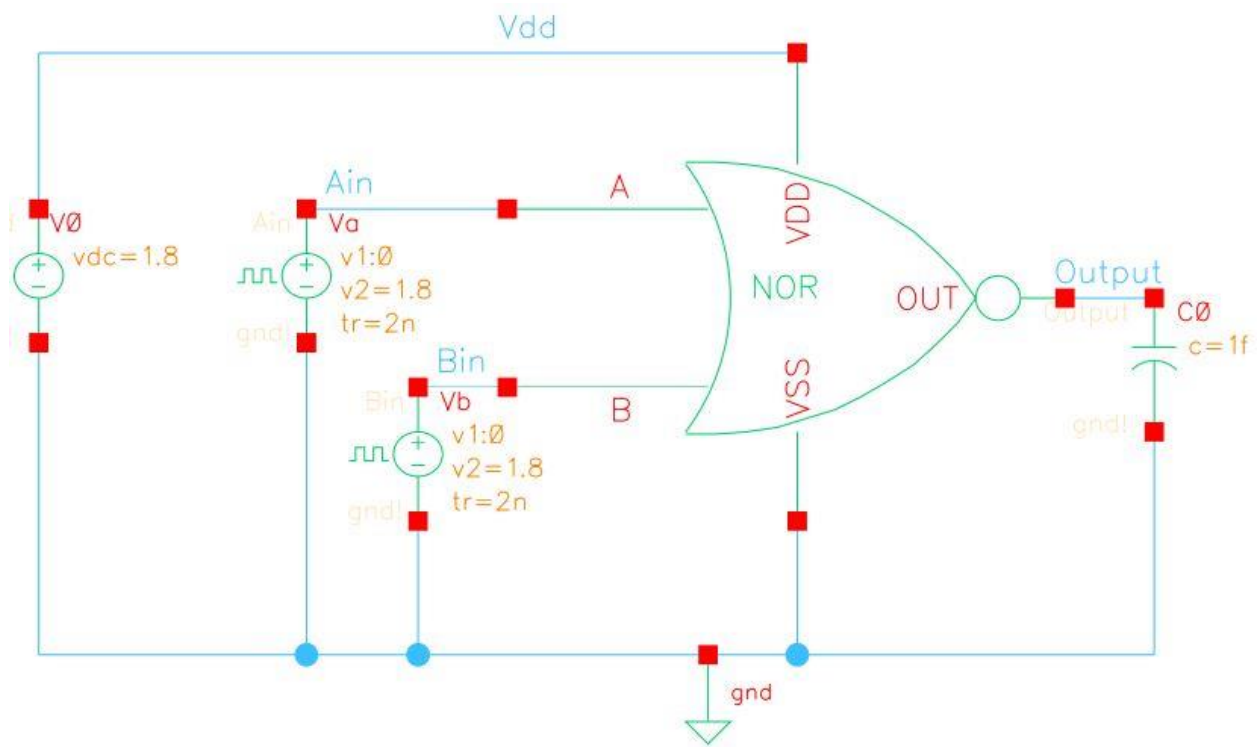


NOR test

Project1:NOR_2_tb:1 : Project1 NOR_2_tb schematic 19:34:19 Thu Mar 8 2018

Transient Response


Thu Mar 8 19:32:57 2018

Name	Vis
/Ain	<input checked="" type="checkbox"/>
/Bin	<input checked="" type="checkbox"/>

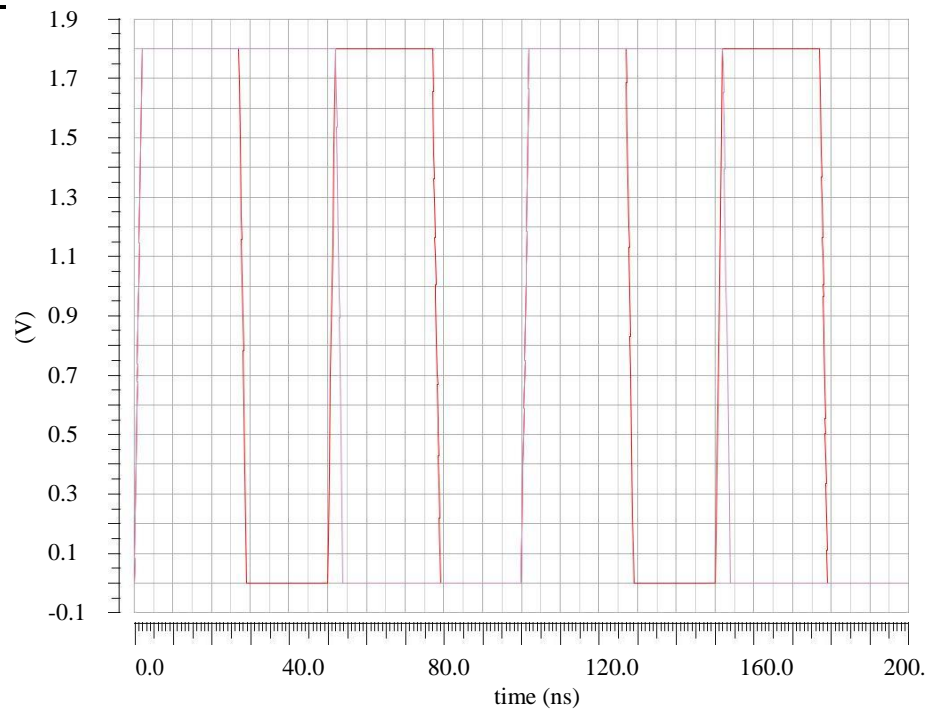

Transient Analysis `tran': time = (0 s -> 200 ns)

Name	Vis
/Output	<input checked="" type="checkbox"/>

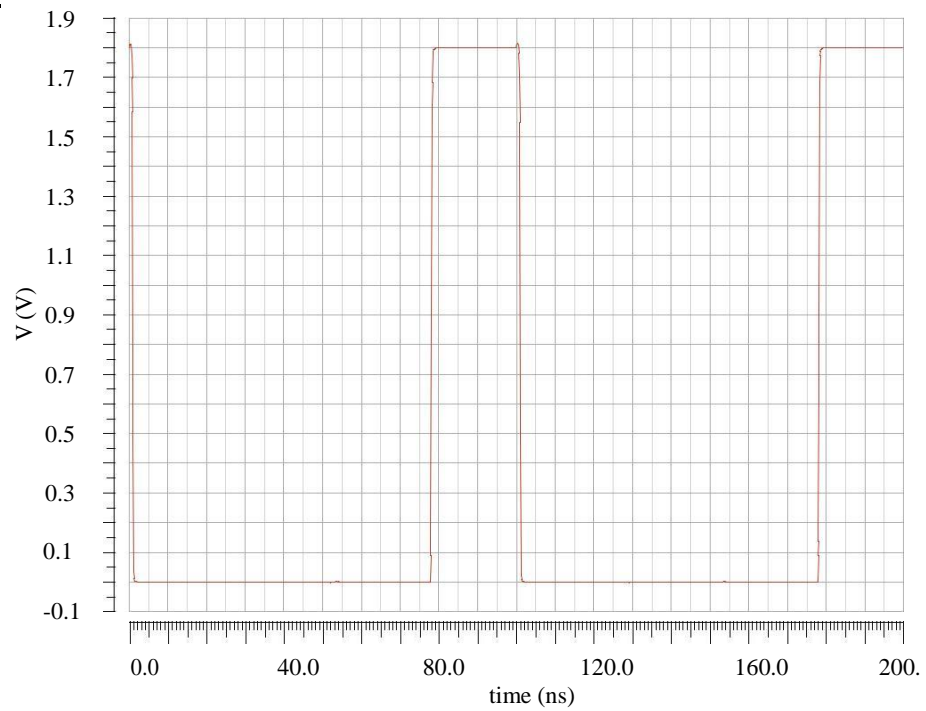


Transmission Gate


$$(W/L)_n = (3.6/0.18)$$

$$(W/L)_p = (7.2/0.18)$$

Schematic (T-Gate)

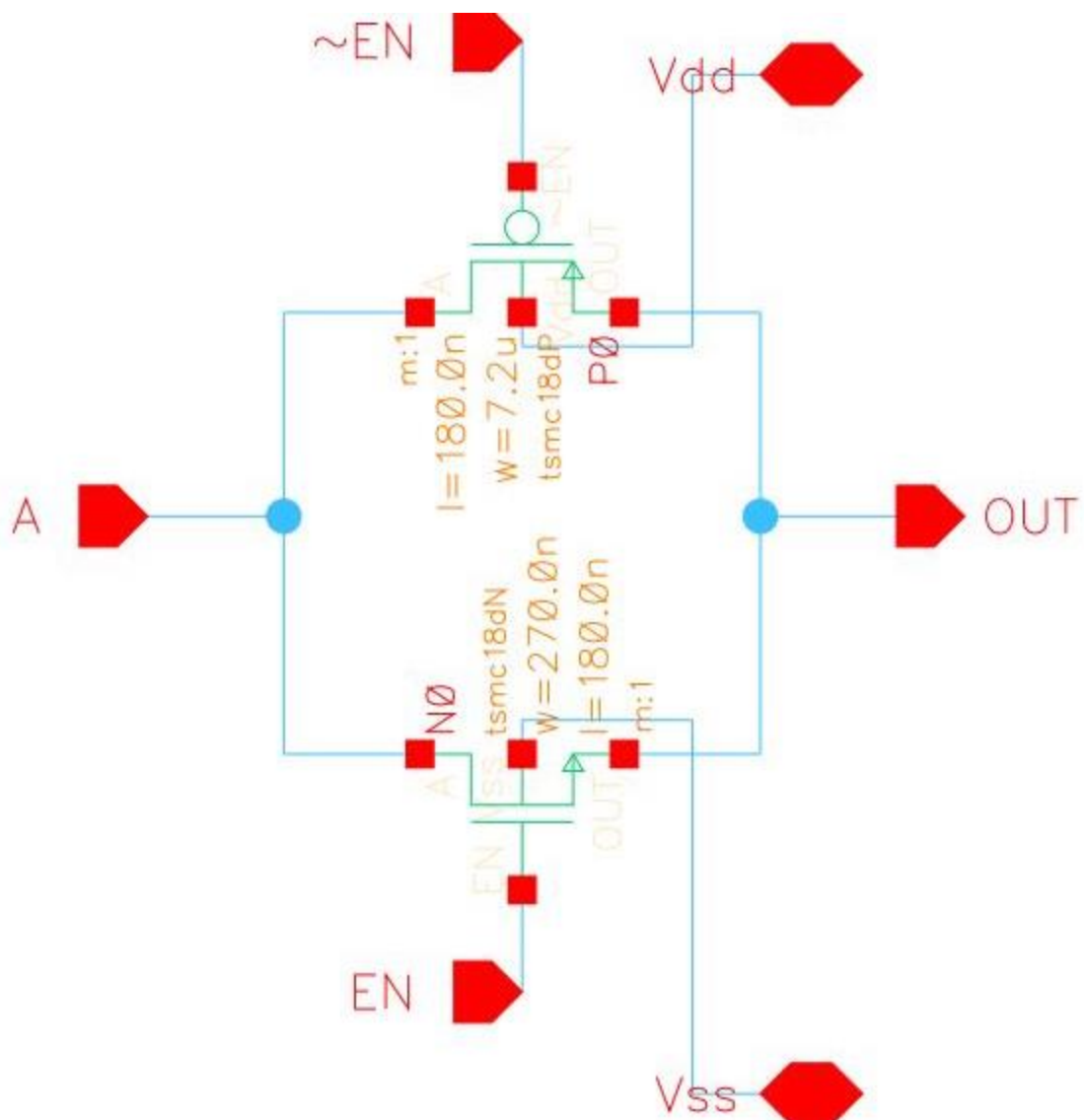

Test-Bench (T-Gate)

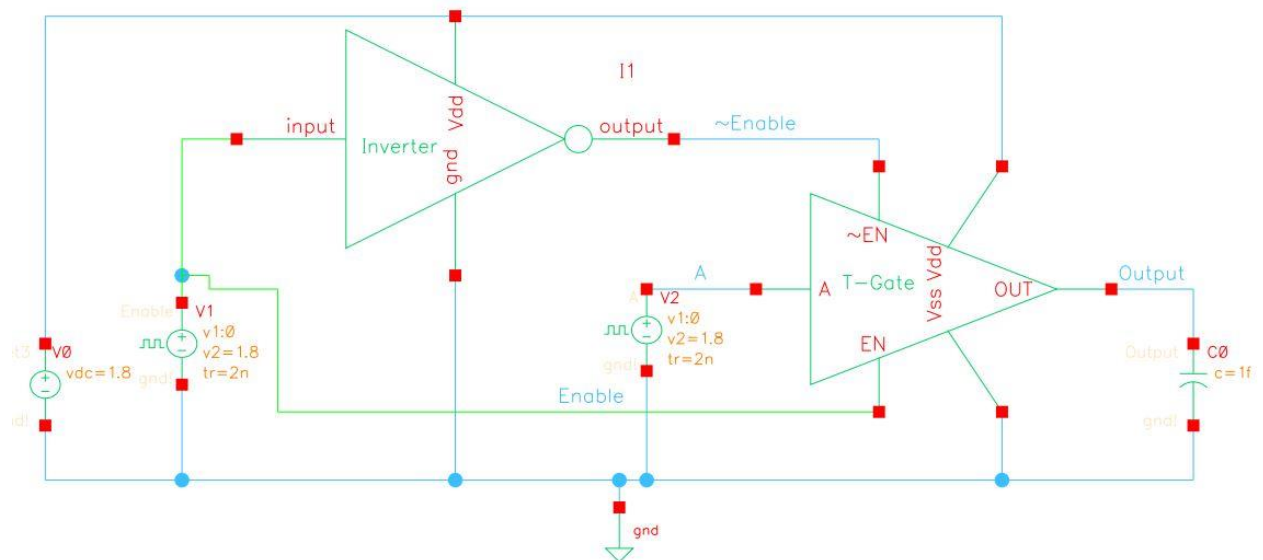


Transmission Gate Test

Project1:T_Gate_tb:1 : Project1 T_Gate_tb schematic 20:28:07 Thu Mar 8 2018

Transient Response


Thu Mar 8 20:27:00 2018

Name	Vis
/~Enable	<input checked="" type="checkbox"/>
/Enable	<input checked="" type="checkbox"/>
/A	<input checked="" type="checkbox"/>

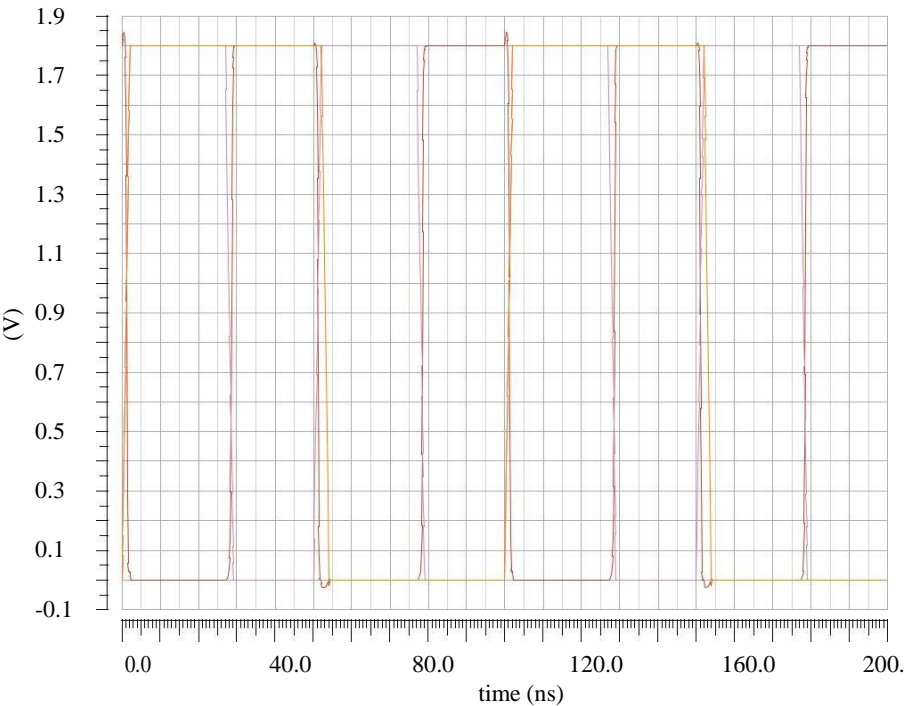


Transient Analysis `tran': time = (0 s -> 200 ns)

Name
/Output

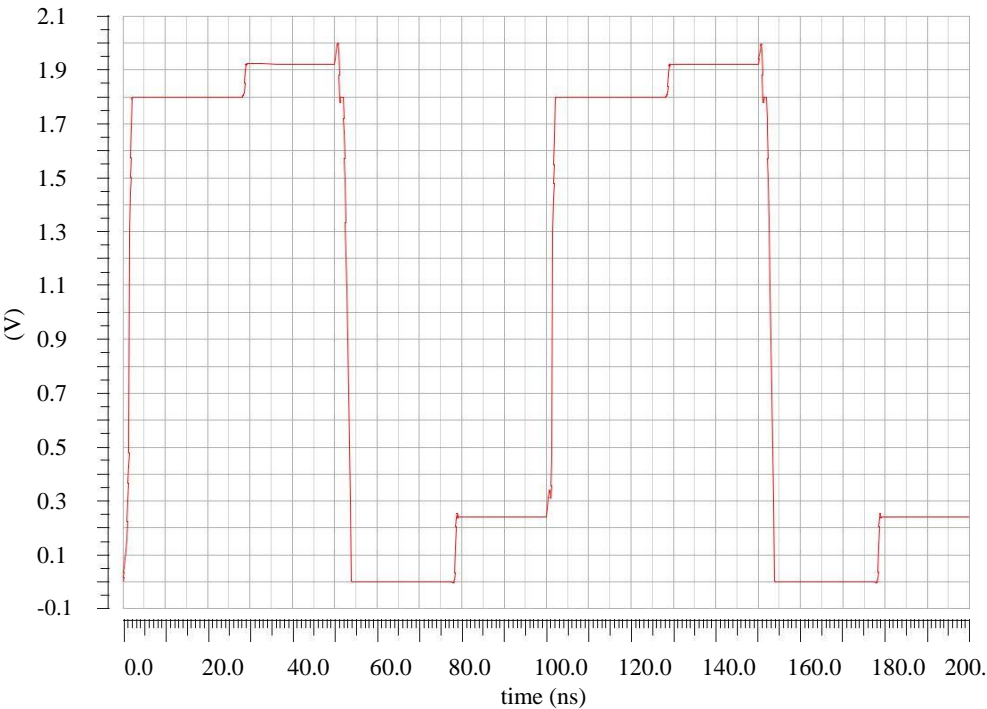


2 – 1 MUX Built out of T-Gates

Schematic (MUX)

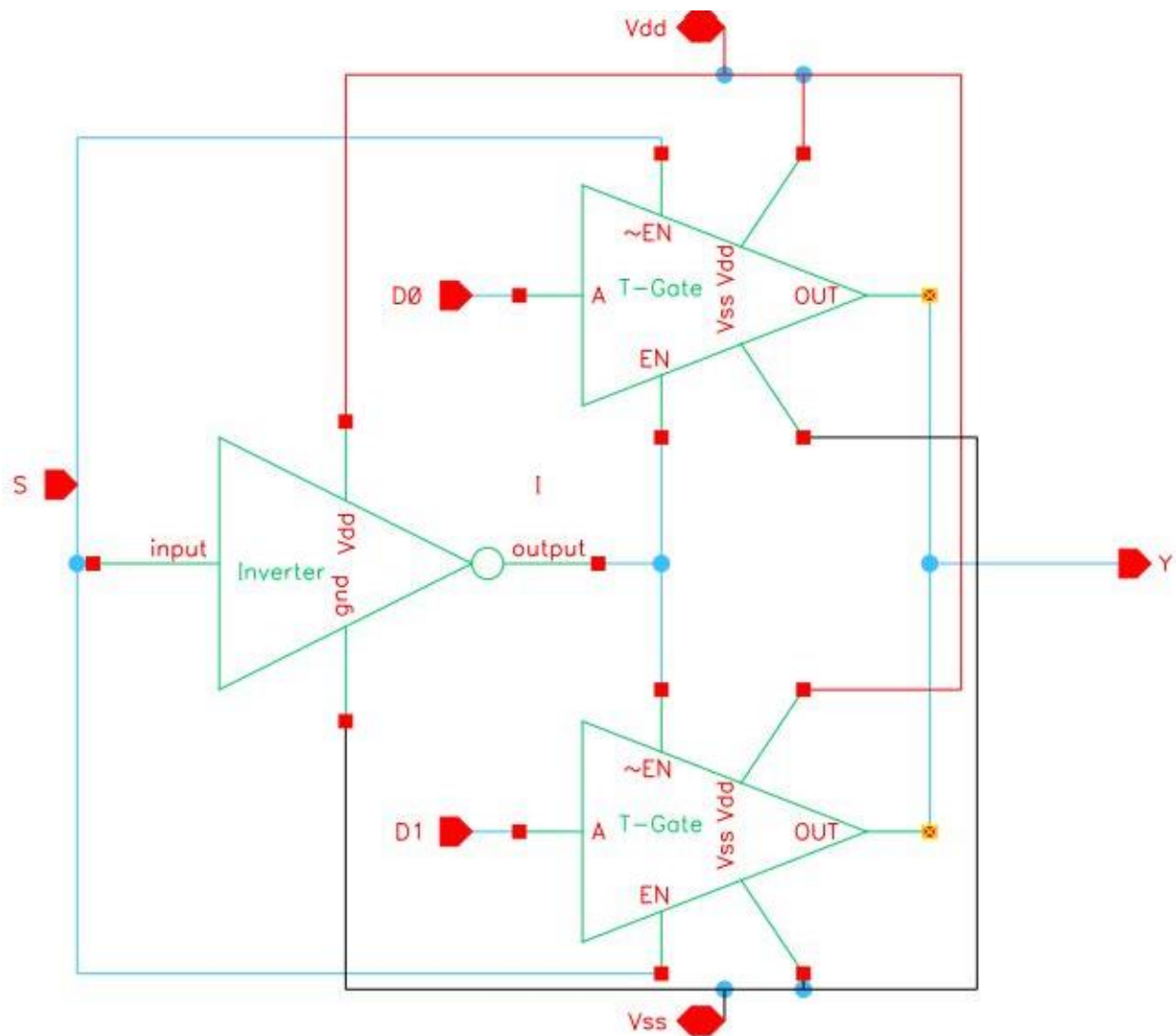


Test-Bench (MUX)

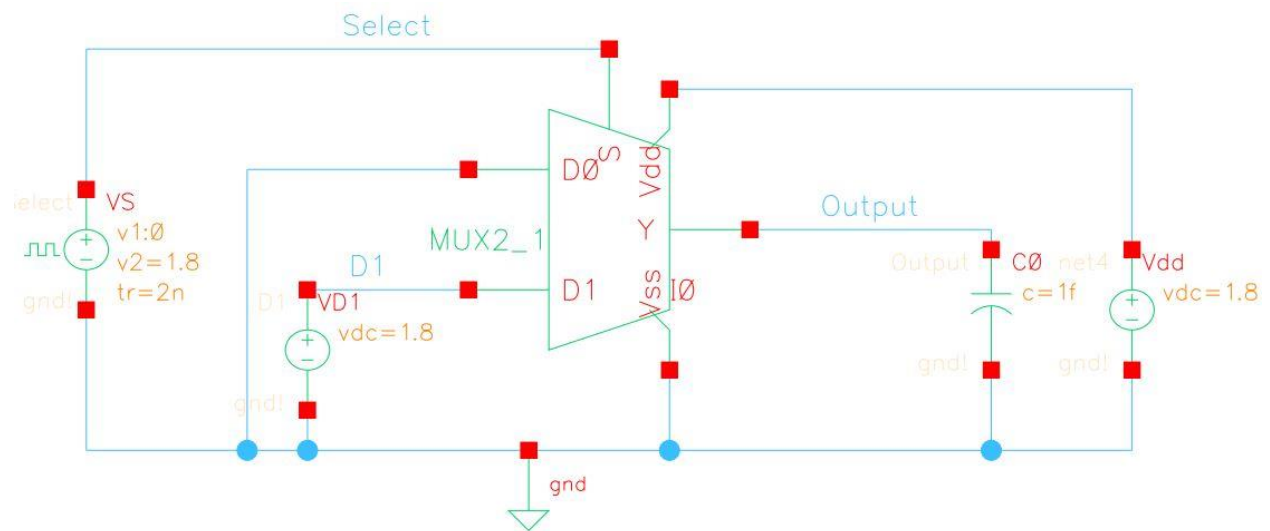

Transient Response

Thu Mar 8 20:37:33 2018

Name	Vis
/D1	
/gnd!	
/Select	

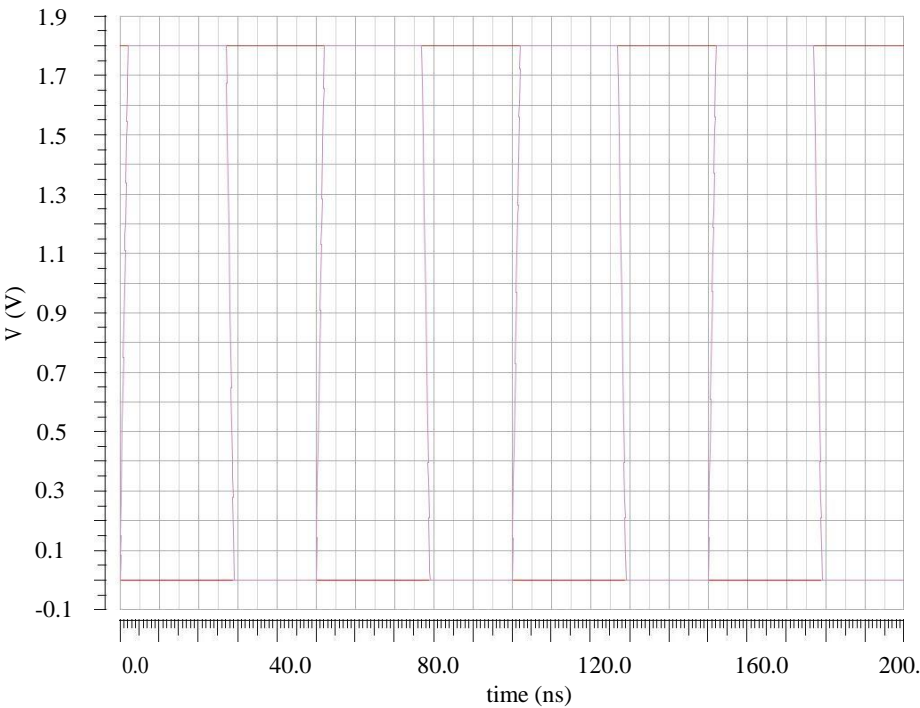

Transient Analysis `tran': time = (0 s -> 200 ns)

Name	Vis
/Output	

